

Name: _____ Date: _____

Collaborators: _____ Lab Section: _____

PRELAB EXERCISES (2 points)

This prelab must be completed and handed in to the lab TA at the start of the lab.

Question 1

1 point

How will you determine the capacitance of the unknown capacitor using the oscilloscope in the first part of the experiment? Explain.

Question 2

1 point

In theory, what should be the slope of the graph you will make of your data when you plot I/Q versus resistance in the second part of the experiment? What value should the y -intercept have?