

Name: _____ Date: _____

Collaborators: _____ Lab Section: _____

POSTLAB EXERCISES (20 points)*Submit the postlab to the TA at the end of the lab.***Ohm's Law (15 points)****Question 3** **$\frac{1}{2}$ point**

Enter the single-resistor data into Data Table 1.

Data table 1: *Single resistor data.* $R =$ _____

Power Supply Setting	Measured Voltage (V)	Measured Current (A)

Question 4 **$\frac{1}{2}$ point**

Enter the light bulb data into Data Table 2.

Data table 2: *Bulb data.*

Power Supply Setting	Measured Voltage (V)	Measured Current (A)

Question 5 **$\frac{1}{2}$ point**

Enter the series resistor data into Data Table 3.

Data table 3: *Series resistor data.*

R_1	
R_2	
V_s	
I_s	
V_1	
V_2	

Question 6 **$\frac{1}{2}$ point**

Enter the parallel resistor data into Data Table 4.


Data table 4: *Parallel resistor data.*

R_1	
R_2	
V_s	
I_s	
I_1	
I_2	

Question 7**2 points**

Single resistor analysis: take the single resistor data from Data Table 1 and plot voltage versus current in Graph 1, including labels and units. Is the relationship linear? If so, draw the best-fit line.

Graph 1: V vs. I for the single resistor.

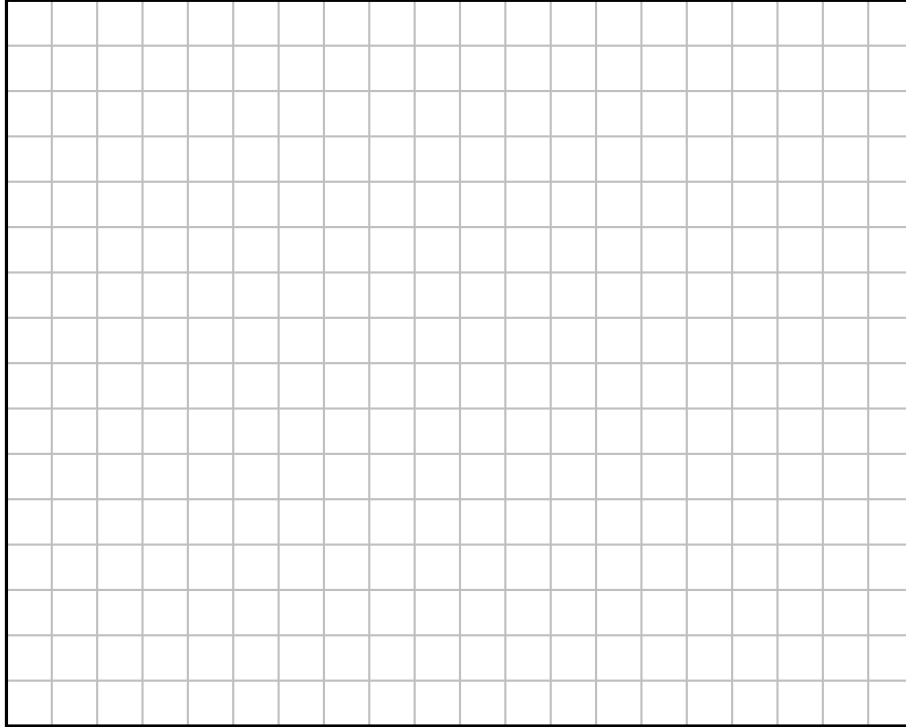**Question 8****1 point**

Calculate the slope of the best-fit line in Graph 1 and use it to estimate the value of R . Compare this to the value labeled on the actual resistor and the value you measured from the multimeter.


Question 9**1 point**

Calculate the power dissipated in the resistor when $V = 6.0$ V.

Question 10**2 points**

Single bulb analysis: take the single resistor data from Data Table 2 and plot voltage versus current in Graph 2, including labels and units.

Graph 2: V vs. I for the light bulb.

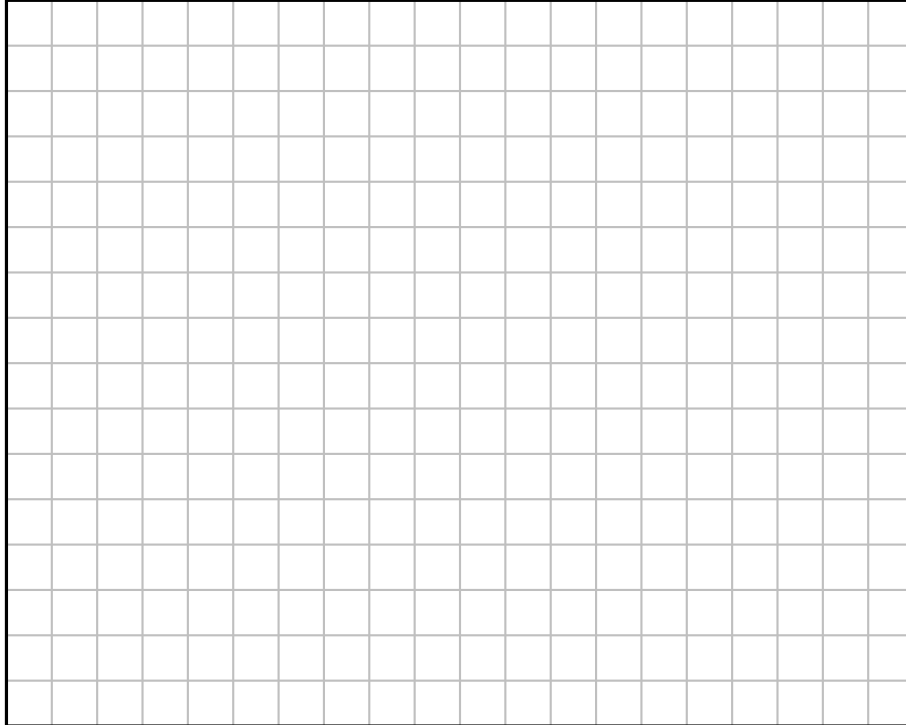**Question 11****1 point**

Is there a linear relationship between voltage and current in Graph 2, compared to the linearity of the single resistor in Graph 1? (It should not be!)

Question 12**1 point**

Calculate the resistance of the filament when $V = 6.0\text{ V}$ and when $V = 1.0\text{ V}$. Note that a non-linear function does not have a constant slope! To calculate the resistance at a certain voltage, draw a line tangent to the curve at that voltage. Then calculate the slope of the tangent line to find the instantaneous resistance.

Question 13**1 point**

Intuitively, do you think the temperature of the filament is higher at $V = 6.0\text{ V}$ and $V = 1.0\text{ V}$? How does this information compare with what you learned about metal superconductors as the temperature decreases?

Question 14**1 point**

Series resistance analysis: Use eq. (4) and verify if your measured V_1 is comparable to the expected value. Show all your work.

Question 15**1 point**

From the value of I_s and V_s , calculate the equivalent or total resistance of the series resistor circuit. Compare this with the theoretical value using eq. (2).

Question 16**1 point**

Parallel resistance analysis: use eq. (5) and verify if your measured I_1 is comparable to the expected value. Show all your work.

Question 17**1 point**

From the value of I_s and V_s , calculate the equivalent or total resistance of the parallel resistor circuit. Compare this with the theoretical value using eq. (3).

Superconductivity (5 points)

Question 18

2 points

Fill in the measurements of the superconducting transition made as the superconductor is allowed to warm up. Use Table 2 to convert the measured thermal conductivity κ in mV to superconductor temperature T in K. Use Ohm's law to convert voltage and current measurements to resistance.

Data table 5: Superconductor Temperature Data.

Thermal Conductivity (mV)	Temperature (K)	Voltage (V)	Current (A)	Resistance (Ω)

Table 2: Conversion of thermal conductivity κ to superconductor temperature T .

κ (mV)	T (K)	κ (mV)	T (K)	κ (mV)	T (K)	κ (mV)	T (K)	κ (mV)	T (K)	κ (mV)	T (K)	κ (mV)	T (K)
6.92	70	6.29	80	5.9	90	5.52	100	5.16	110	4.81	120	4.46	130
6.85	71	6.25	81	5.86	91	5.48	101	5.13	111	4.77	121	4.42	131
6.78	72	6.21	82	5.83	92	5.44	102	5.09	112	4.74	122	4.39	132
6.71	73	6.17	83	5.79	93	5.41	103	5.06	113	4.70	123	4.35	133
6.64	74	6.13	84	5.75	94	5.37	104	5.02	114	4.67	124	4.32	134
6.56	75	6.09	85	5.72	95	5.34	105	4.99	115	4.63	125	4.28	135
6.49	76	6.05	86	5.68	96	5.30	106	4.95	116	4.60	126	4.25	136
6.42	77	6.01	87	5.64	97	5.27	107	4.91	117	4.56	127	4.21	137
6.37	78	5.97	88	5.6	98	5.23	108	4.88	118	4.53	128	4.18	138
6.33	79	5.93	89	5.56	99	5.20	109	4.84	119	4.49	129	4.14	139

Question 19**3 points**

Take your measurements from Data Table 5 and plot of resistance versus temperature in Graph 3. Include labels and units. Do not draw a line of best fit. Mark on your plot the temperature where the levitating magnet fell. What is the critical temperature T_C of the superconductor?

Graph 3: R vs. T for the Superconductor.

